

Homework Solutions -1

Solution 1.18

$$p_1 = 30(-10) = \mathbf{-300 \text{ W}}$$

$$p_2 = 10(10) = \mathbf{100 \text{ W}}$$

$$p_3 = 20(14) = \mathbf{280 \text{ W}}$$

$$p_4 = 8(-4) = \mathbf{-32 \text{ W}}$$

$$p_5 = 12(-4) = \mathbf{-48 \text{ W}}$$

Solution 1.20

$$p_{30 \text{ volt source}} = 30 \times (-6) = \mathbf{-180 \text{ W}}$$

$$p_{12 \text{ volt element}} = 12 \times 6 = \mathbf{72 \text{ W}}$$

$$p_{28 \text{ volt element with 2 amps flowing through it}} = 28 \times 2 = \mathbf{56 \text{ W}}$$

$$p_{28 \text{ volt element with 1 amp flowing through it}} = 28 \times 1 = \mathbf{28 \text{ W}}$$

$$p_{\text{the } 5I_o \text{ dependent source}} = 5 \times 2 \times (-3) = \mathbf{-30 \text{ W}}$$

Since the total power absorbed by all the elements in the circuit must equal zero,
or $0 = -180 + 72 + 56 + 28 - 30 + p_{\text{into the element with } V_o}$ or


$$p_{\text{into the element with } V_o} = 180 - 72 - 56 - 28 + 30 = \mathbf{54 \text{ W}}$$

Since $p_{\text{into the element with } V_o} = V_o \times 3 = 54 \text{ W}$ or $V_o = \mathbf{18 \text{ V}}$.

Solution 1.26

- (a) Clearly $10.78 \text{ watt-hours} = (\text{voltage})(\text{current})(\text{time}) = 3.85I(3) \text{ or}$
 $I = 10.78/[(3.85)(3)] = \mathbf{933.3 \text{ mA}}$
- (b) $p = \text{energy}/\text{time} = 10.78/3 = \mathbf{3.593 \text{ W}}$
- (c) $\text{amp-hours} = \text{energy}/\text{voltage} = 10.78/3.85 = \mathbf{2.8 \text{ amp-hours}}$

Solution 2.14

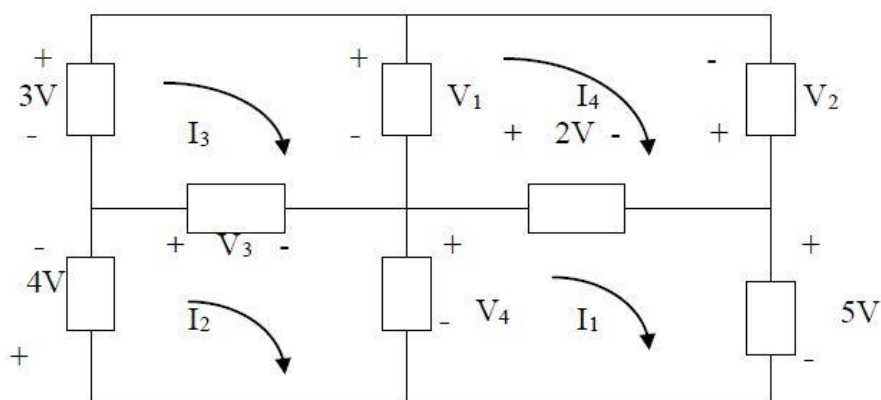

For mesh 1,

$$-V_4 + 2 + 5 = 0 \longrightarrow V_4 = 7V$$

For mesh 2,

$$+4 + V_3 + V_4 = 0 \longrightarrow V_3 = -4 - 7 = -11V$$

For mesh 3,

$$-3 + V_1 - V_3 = 0 \longrightarrow V_1 = V_3 + 3 = -8V$$

For mesh 4,

$$-V_1 - V_2 - 2 = 0 \longrightarrow V_2 = -V_1 - 2 = 6V$$

Thus,

$$\underline{V_1 = -8V, \quad V_2 = 6V, \quad V_3 = -11V, \quad V_4 = 7V}$$

Solution 2.15

Calculate v and i_x in the circuit of Fig. 2.79.

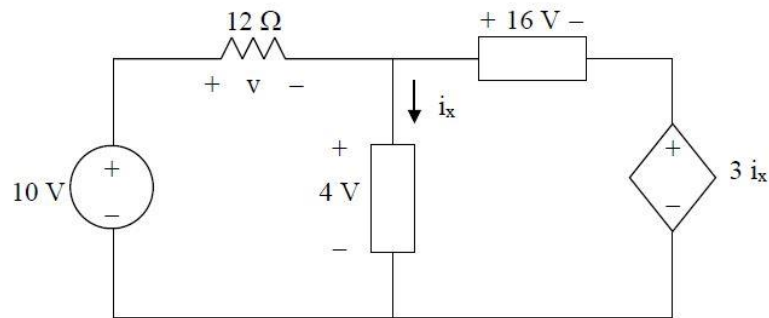


Figure 2.79
For Prob. 2.15.

Solution

For loop 1, $-10 + v + 4 = 0$, $v = \mathbf{6\text{ V}}$

For loop 2, $-4 + 16 + 3i_x = 0$, $i_x = \mathbf{-4\text{ A}}$

Applying KVL around the entire outside loop we get,

$$-24 + v_1 + 10 + 12 = 0 \text{ or } v_1 = \mathbf{2V}$$

Applying KVL around the loop containing v_2 , the 10-volt source, and the 12-volt source we get,

$$v_2 + 10 + 12 = 0 \text{ or } v_2 = \mathbf{-22V}$$

Applying KVL around the loop containing v_3 and the 10-volt source we get,

$$-v_3 + 10 = 0 \text{ or } v_3 = \mathbf{10V}$$